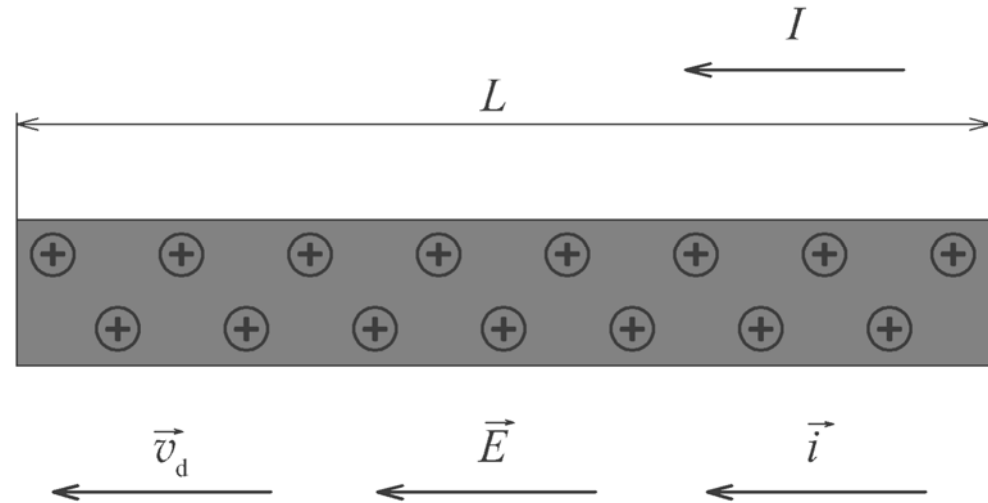


Electric current



Electric current

$$I = \frac{dQ}{dt}$$



drift velocity \vec{v}_d

current density $dI = \vec{i} \cdot d\vec{S}$

$$I = \frac{Q}{\tau} = \frac{nSLe}{\frac{L}{v_d}} = nSev_d$$

$$i = nev_d$$

$$\vec{i} = ne\vec{v}_d$$

$$Q = Ne = nSLe$$

$$N = nSL$$

Ohm's law

$$U = RI$$

$$R = \rho \frac{l}{S}$$

$$\rho = \frac{1}{\gamma}$$

$$\Delta U = \varphi_1 - \varphi_2 = \vec{E} \cdot \Delta \vec{l}$$

$$\vec{i} = \gamma \vec{E}$$

conductors

$$10^{-7} - 10^{-8} \, \Omega \cdot \text{m}$$

non-conductors

$$10^6 - 10^{16} \, \Omega \cdot \text{m}$$

semiconductors

$$10^{-6} - 10^7 \, \Omega \cdot \text{m}$$

linear temperature function

$$R = R_0 \left[1 + \alpha (t - t_0) \right]$$


“emf” and “emf device”

$$\vec{E}^* = \frac{\vec{F}^*}{Q}$$

electromotive force

emf device
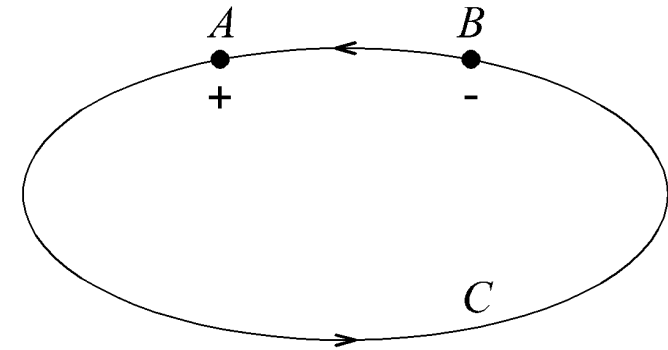
$$U_{AB} = \int_A^B \vec{E}_s \cdot d\vec{l}$$



$$\oint_C \vec{E} \cdot d\vec{l} = \int_{AB} \vec{E}_s \cdot d\vec{l} + \int_{BA} (\vec{E}_s + \vec{E}^*) \cdot d\vec{l} = \int_{AB} \vec{E}_s \cdot d\vec{l} + \int_{BA} \vec{E}_s \cdot d\vec{l} + \int_{BA} \vec{E}^* \cdot d\vec{l}$$

$$\int_{AB} \vec{E}_s \cdot d\vec{l} + \int_{BA} \vec{E}_s \cdot d\vec{l} = \oint_C \vec{E}_s \cdot d\vec{l} = 0$$

$$\int_{AB} \vec{E}_s \cdot d\vec{l} = - \int_{BA} \vec{E}_s \cdot d\vec{l} = U_{AB}$$

$$\mathcal{E} = \int_{BA} \vec{E}^* \cdot d\vec{l}$$

$$\oint_C \vec{E} \cdot d\vec{l} = \int_{BA} \vec{E}^* \cdot d\vec{l}$$

energy per unit charge = **emf**

= potential (\approx voltage)

$$I = \frac{U_{AB}}{R} = \frac{1}{R} \int_{AB} \vec{E}_s \cdot d\vec{l}$$

$$I = \frac{1}{R_i} \int_{BA} (\vec{E}_s + \vec{E}^*) \cdot d\vec{l} = \frac{1}{R_i} \int_{BA} \vec{E}_s \cdot d\vec{l} + \frac{1}{R_i} \int_{BA} \vec{E}^* \cdot d\vec{l} = -\frac{RI}{R_i} + \frac{\mathcal{E}}{R_i}$$

$$\int_{AB} \vec{E}_s \cdot d\vec{l} = RI$$

$$\mathcal{E} = (R + R_i)I$$


$$\mathcal{E} = U_{AB} + R_i I \quad \text{terminal voltage}$$

Kirchhoff's laws

1st Kirchhoff's law (current rule)

The algebraic sum of currents in a network of conductors meeting at a point is zero.


$$\sum_{k=1}^N I_k = 0$$

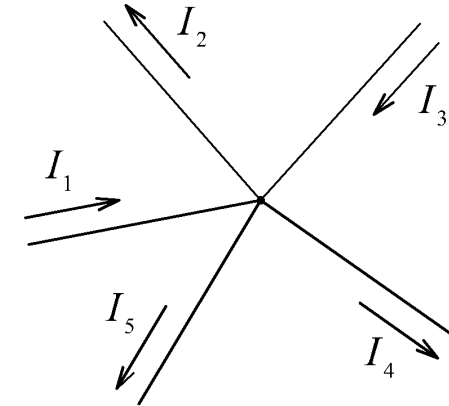

2nd Kirchhoff's law (voltage rule)

The directed sum of the potential differences (voltages) around any closed loop is zero.
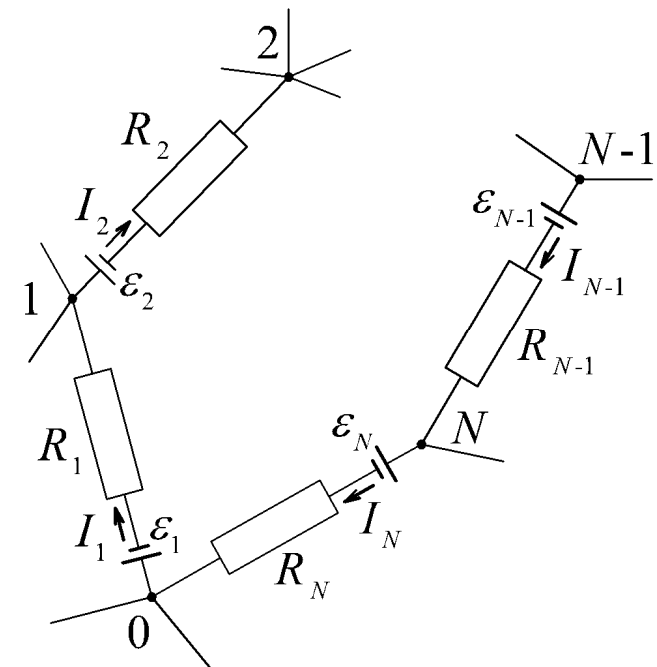
$$\sum_{k=1}^N \mathcal{E}_k = \sum_{k=1}^N R_k I_k$$



Energy and power in circuits

HRW: Ch27

$$dW_p = dQ \quad U = I dt U$$

Joule's law (Joule heating):

the heat power that develops in a wire carrying a current is proportional to the wire resistance the square of the current.

$$P = UI \quad P = \frac{U^2}{R}, \quad P = RI^2$$

$$p = \vec{E} \cdot \vec{i} \quad \text{differential Joule's law}$$

$$p = \frac{dP}{dV} \quad \text{heat power density}$$

energy per unit time τ

$$W = \int_0^t P d\tau = \int_0^t UI d\tau = \int_0^t U dQ$$

Thermoelectric effect



- Intrinsic connection of charge and heat transport phenomena
- A matter subjected to temperature gradient = diffusion of carriers

Seebeck effect $T_1 \neq T_2$

$$I = \frac{U_{AB}(T_1) - U_{AB}(T_2)}{R}$$

$$\mathcal{E}_k = U_{AB}(T_1) - U_{AB}(T_2)$$

thermocouple principle

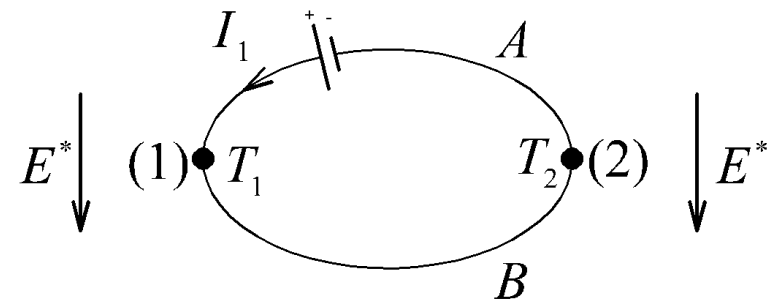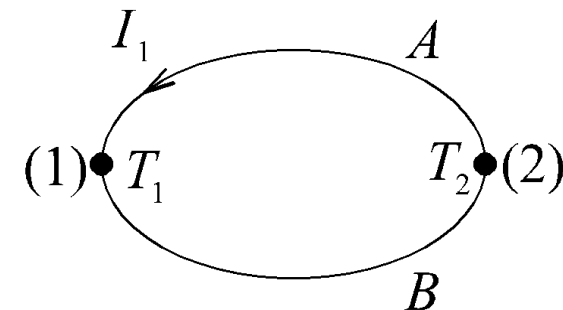

Peltier effect $T_2 > T_1$

inverse to Seebeck effect – thermoelectric pumps (cooling, heating)